

[Home](#) / [Electronics](#) / [Circuit Design](#) / [Current Sensing](#)

Current Sensing


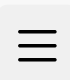

Article by: [Geoffrey Hunter](#)

Date Published: *August 20, 2012*

Last Modified: *September 16, 2023*

1. Low-Side Resistive Current Sensing

One of the most basic ways to measure current is to use a low-side current sensing

-  mbedded.ninja
-
- 
- Simple and cheap
 - Single-ended output due to resistor being on the low-side. This means you can feed a single signal into a ADC (because it is referenced to GND).

TIP

High-side current-sense resistors require differential measurements.

[Figure 1](#) shows the oscilloscope the voltage on the top-side of a low-side 100mΩ resistor connected to a small brushed DC motor as it is turned on. The voltage peaks at 280mV, which corresponds to 2.8A ($I = \frac{V}{R}$). It then drops and settles down to approx. 90mV, which corresponds to 0.9A. I think the noise is due to the switching action of the motors brushes.


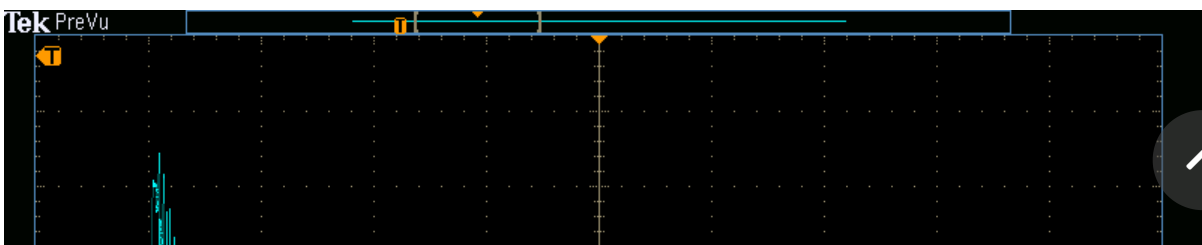
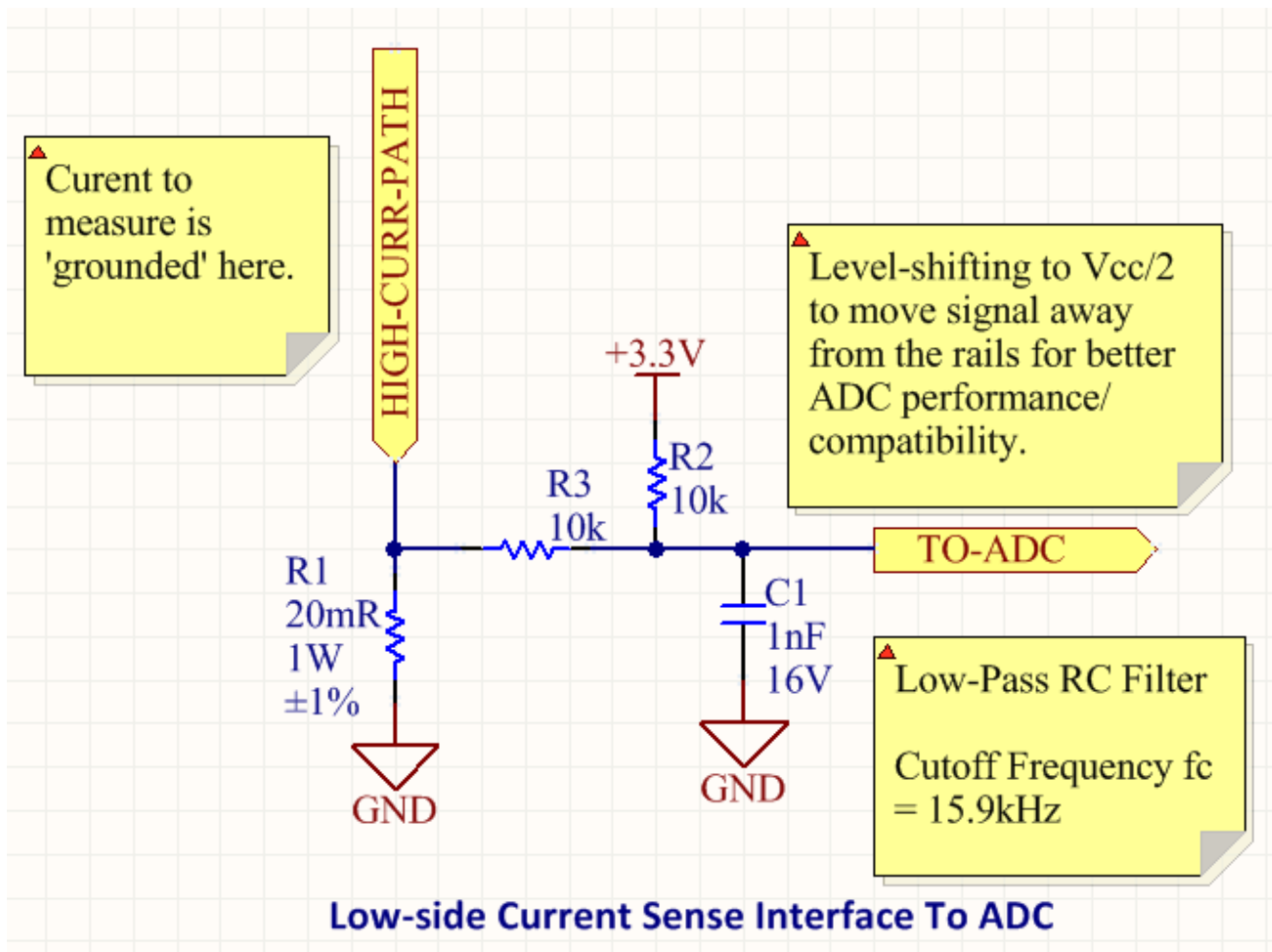


Figure 1: Oscilloscope capture of the voltage across a low-side $100\text{m}\Omega$ resistor connected to a small brushed DC motor.

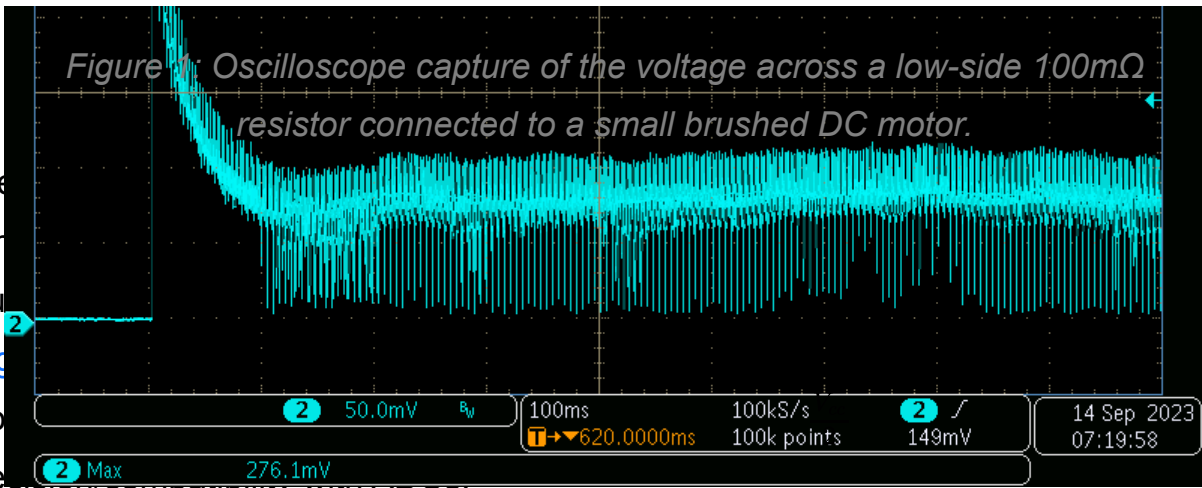

A schematic for a low-side current sensing circuit that can be connected to a microcontroller/MCU ADC.

The value of the resistance is a trade-off between resolution and power dissipation/circuit disruption. The higher the current-sense resistance, the larger the voltage signal for a given current and hence better resolution. However, a larger voltage means both more power dissipation in the resistance AND greater disruption to the circuit you are trying to measure. Assuming a resistive load, disruption means the load begins to see a reduced voltage and draws less current (the very current you are trying to measure!).

Generally speaking, choosing a resistance that drops a few hundred of millivolts at max. current is a good starting point. This voltage can be fed directly into a MCU ADC if you just want a rough current measurement, or can be pass through a [op-amp amplifier stage](#) first to increase the full-scale range.

Another thing to consider is whether or not you need **Kelvin sensing**. If you just take a **single tap of the top-side of the resistor** to your ADC, you are measuring the voltage **drop across the resistor AND the ground plane** between the resistor and the ADC. This drop across the ground plane **could introduce a significant error in your measurement if the resistance of the current sense resistor is in the same order of magnitude as the ground plane resistance**. To compensate for this you can perform **Kelvin sensing (four-terminal sensing)** by taking separate feeds back to the ADC from both the top and bottom of the resistor, however this will require a **differential measurement**.

Authors



Geoffrey Hunter

Dude making stuff.

 [Twitter](#)

 [GitHub](#)



Support Me on Ko-fi



This work is licensed under a [Creative Commons Attribution 4.0 International License](#).

Related Content

- [Four Terminal \(4T\) Sensing](#)

Tags

- [current sensing](#)

